Simple Circuit

−   +

Tape LED to Top of Copper Tape

← **Copper Tape**

Battery on Top of Copper Tape w/ Negative (-) Facing Down

−

Fold Line →

+