Series Circuit

-   LED   +   -   LED   +

Tape LEDs to Top of Copper Tape

← **Copper Tape**

(2) Coin Cell Batteries on Top of Copper Tape w/ Negatives (-) Facing Down

↓

−

Fold Line →

+